

COMS12200 problem set #6

Within this problem slot, the idea is that you attempt to solve the set of pencil-and-paper, exam-style questions presented below; in doing so, you can (optionally) use an interactive system to anonymously register your solutions. More concretely, optionally start by installing the Socrative client, e.g.,

- for Chrome

<http://chrome.google.com/webstore/detail/socrative-student/nblhpecglllndfihpmpdoikimcmgkha>

- for Android

<http://play.google.com/store/apps/details?id=com.socrative.student>

- for iOS

<http://itunes.apple.com/gb/app/socrative-student/id477618130>


or using the web-based application at

<http://www.socrative.com>,


then entering the 9-character “room name” which should be displayed top-center on the projector screen. Then, we will alternate as follows:

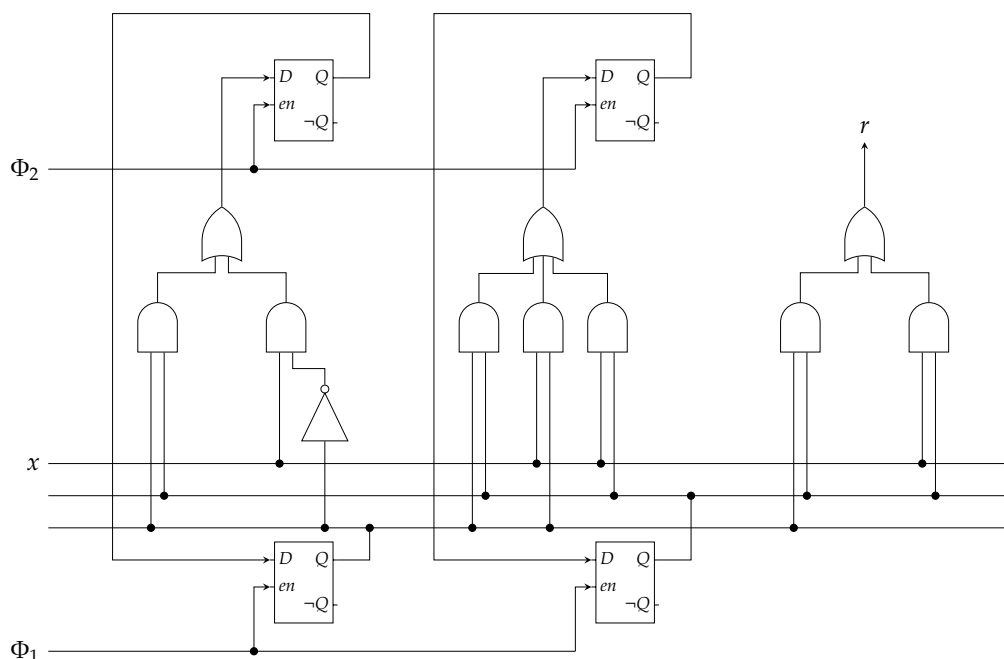1. solve the current question, and optionally register your solution using Socrative,
2. wait until everyone is finished (or say ~ 5 minutes elapse), at which point we will discuss the questions and solutions using any collated Socrative results as a starting point.

All questions in this Section relate to a Finite State Machine (FSM) whose concrete implementation is as follows:



 Notice that the implementation is based on use of four D-type latches, and a 2-phase clock supplied via Φ_1 and Φ_2 ; one additional input x plus one output r are also evident. To function correctly, a clock generator ensures Φ_1 and Φ_2 are driven as follows:



Q1. From the following list


- A: Φ_1 and Φ_2 are digital signals
- B: Φ_1 and Φ_2 are non-overlapping
- C: Φ_1 and Φ_2 are gated
- D: Φ_1 and Φ_2 are unskewed
- E: Φ_1 and Φ_2 each have a duty cycle of 33%

identify **each** property the clock generator *must* guarantee is true for the implementation to function correctly.

Q2. Consider the two D-type latches at the bottom of the diagram, which form a 2-bit register. Imagine the value stored in this register is expressed as a 2-bit integer: when the implementation is initially powered-on, is this value equal to

- A: $00_{(2)}$
- B: $01_{(2)}$
- C: $10_{(2)}$
- D: $11_{(2)}$
- E: any of the above

 Q3. Any FSM specification will include a transition function, often denoted δ , which can be described in either tabular or diagrammatic form. Of the following options



which captures the transition function of this FSM?

- Q4.** Which of the following FSM types, namely
- A: Mealy
 - B: Moore
- does this implementation represent?
- Q5.** In the 2-phase clock waveform above, ρ illustrates the clock period: recall this is inversely proportional to the clock frequency. Imagine the gate delay for NOT, AND, and 2- and 3-input OR gates are 10ns 20ns 20ns, 30ns respectively, and the critical path associated for a D-type latch is 60ns. Which of the following best matches the maximum possible clock frequency of this implementation?
- A: 1.0kHz
 - B: 5.9MHz
 - C: 9.0MHz
 - D: 9.5MHz
 - E: 1.0GHz
- Q6.** Which of the following best describes the purpose of this FSM?
- A: set $r = 1$ iff. the current value of x is different from the previous value of x ,
 - B: act as a modulo 4 counter that is incremented by the value of x , and set $r = 1$ the current counter value is zero,
 - C: compute the Hamming weight of a sequence fed as input bit-by-bit via x , and set $r = 1$ once this is equal to 3
 - D: count the number of consecutive times $x = 1$, and set $r = 1$ once this is equal to 3
 - E: inspect the sequence fed as input bit-by-bit via x , and set $r = 1$ iff. this sequence, when interpreted as an unsigned integer, is odd